

Roll No.

Total Pages : 3

OBCAM-15

19004

LOGICAL ORGANIZATION OF COMPUTERS

Paper-BCA-104

Time Allowed : 3 Hours]

[Maximum Marks : 80

Note : Attempt **five** questions in all, selecting at least **one** question from each Unit. Question No. 1 is compulsory. All questions carry equal marks.

Compulsory Question

1. (a) Find the complement of the Boolean function
 $F = X \cdot \bar{Y} + \bar{X} \cdot Z \cdot (\bar{X} + Y)$.
- (b) Draw the logic diagram of D type Flip-Flop.
- (c) Differentiate between Primary memory and Secondary memory.
- (d) What is meant by Instruction cycle?
- (e) What is the function of IOP? 4,3,3,3,3

UNIT-I

2. (a) What are Self complementing codes? Give example.
- (b) What are Cyclic or Gray codes?
- (c) Explain the methods of detecting errors during data transmission. 4,5,7

19004/K/733/250

P. T. O.

3. (a) Prove following theorems using Boolean Algebra postulates :

(i) $a + a = 9$

(ii) $a - a = 9$

(iii) $a + 1 = 1$

- (b) Simplify the Boolean function using K-map.

$$F(A, B, C, D) = \sum(0, 2, 3, 7, 9) + \sum_{\phi}(1, 5, 11, 14).$$

9, 7

UNIT-II

4. (a) Design and Implement Full adder circuit.
 (b) What is Multiplexer? Design a 4×1 multiplexer.
 9, 7
5. Design and Implement BCD to Excess-3 code converter.
 16

UNIT-III

6. (a) Draw the logic diagram of J-K Flip-Flop, its characteristic table and characteristic equation and explain its working.
 (b) What is Race condition in J-K Flip-Flop? What are the methods of removing it?
 10, 6
7. (a) Draw the logic diagram of Parallel-In Serial-out Register and explain its working.
 (b) Design a mod-5 counter.
 8, 8

19004/K/733/250

2

UNIT-IV

8. Define Instruction Format? Explain the various Instruction formats giving example.
 16
9. Explain the Program controlled and Interrupt controlled data transfer.
 16

19004/K/733/250

3